
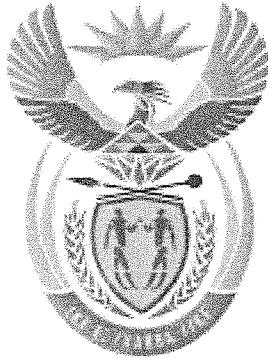


0000000000

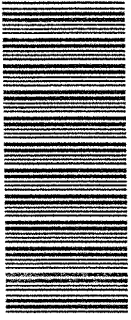

# higher education & training

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

T490(E)(A13)T  
APRIL EXAMINATION

**NATIONAL CERTIFICATE**

**ELECTROTECHNICS N4**

(8080074)

**13 April 2015 (Y-Paper)**  
**13:00–16:00**

**REQUIREMENTS:** Graph paper

Calculators may be used.

This question paper consists of 6 pages and 1 formula sheet of 2 pages.

**DEPARTMENT OF HIGHER EDUCATION AND TRAINING**  
**REPUBLIC OF SOUTH AFRICA**  
NATIONAL CERTIFICATE  
ELECTROTECHNICS N4  
TIME: 3 HOURS  
MARKS: 100

---

**INSTRUCTIONS AND INFORMATION**

1. Answer ALL the questions.
  2. Read ALL the questions carefully.
  3. Number the answers according to the numbering system used in this question paper.
  4. Write neatly and legibly.
-

**QUESTION 1**

- 1.1 The field coil of a motor has a resistance of  $300 \Omega$  at  $75^\circ\text{C}$ .  
Calculate the final resistance if the temperature is  $200^\circ\text{C}$ . Take the temperature coefficient of resistance as  $0,004^\circ\text{C}$  at  $75^\circ\text{C}$ . (4)
- 1.2 Distinguish between a positive and a negative temperature coefficient of resistance. (3)
- 1.3 A coil having 1 500 turns of conductor with a combined cross-sectional area of  $300 \text{ mm}^2$  and a mean length per turn of  $400 \text{ mm}$ , has an inductance of  $3 \text{ H}$ .  
Calculate the following:
- 1.3.1 The resistance of the winding if the resistivity (specific resistance) of the conductor is  $4 \mu\Omega\cdot\text{m}$  (5)
- 1.3.2 The average value of the EMF induced in the coil when a current of  $60 \text{ A}$  reversed in  $15 \text{ seconds}$  (2)
- 1.4 Two capacitors connected in series have voltage readings of  $40 \text{ V}$  and  $10 \text{ V}$  respectively. The total charge equals  $400 \mu\text{C}$ .  
Calculate the following:
- 1.4.1 The total capacitance (2)
- 1.4.2 The value of each capacitor (4)
- [20]

**QUESTION 2**

- 2.1 Explain Kirchhoff's first law. (2)
- 2.2 Two batteries of EMF  $65 \text{ V}$  and  $50 \text{ V}$  and internal resistance of  $0,3 \Omega$  and  $0,6 \Omega$  respectively, are connected in parallel to supply a load resistance of  $2,8 \Omega$ .  
Use Kirchhoff 's laws and calculate the following:
- 2.2.1 The current supplied by each battery (7)
- 2.2.2 The voltage across the load (2)
- 2.3 Define a *farad*. (3)

2.4 A resistor of unknown value  $R$  is connected in parallel with a resistance of  $180 \Omega$ . This combination is connected in series with a resistance of  $25 \Omega$ . The circuit is then connected across a  $280\text{-V}$  DC-supply.

Calculate the following:

2.4.1 The value of the resistor  $R$  when a  $4\text{-A}$  current is drawn from the supply (5)

2.4.2 The power dissipated in the circuit (1)

[20]

### QUESTION 3

3.1 The open-circuit characteristics of a shunt-excited DC motor are as follow:

Terminal voltage (V)	200	400	500	580	610	620
Field current (A)	10	20	30	50	65	75

Using the above values, plot a graph and determine the following:

3.1.1 The voltage which the motor will excite on no-load when shunt connected if the total field resistance is  $10 \Omega$ . (8)

3.1.2 The critical resistance (2)

3.2 A long-shunt compound-wound DC motor has an armature resistance of  $0,3 \Omega$ , a series-field resistance of  $0,1 \Omega$  and a shunt-field resistance of  $48 \Omega$ . The motor draws a current of  $210 \text{ A}$  from a  $480\text{-V}$  DC supply.

Calculate the EMF generated in the armature. (5)

3.3 What is the purpose of a pole shoe in a DC motor? (2)

3.4 Name any THREE types of capacitors. (3)

[20]

**QUESTION 4**

4.1 What can be done to improve the power factor in a circuit? (2)

4.2 A 50 Hz sinusoidal voltage has an RMS value of 424,2 V.

Calculate the following:

4.2.1 The time for the voltage to reach a value of 300 V from zero for the first time (4)

4.2.2 Draw a phasor diagram and show the waveform of this voltage. (2)

4.3 A coil with a resistance of 200  $\Omega$  and an inductance of 0,3183 H is connected in series with a 10,61- $\mu$ f capacitor. This circuit is connected across a 565/-685 V, 50 Hz supply.

Calculate the voltage drop across the following:

4.3.1 The coil (7)

4.3.2 The capacitor (1)

4.3.3 Draw the phasor diagram to represent the distribution of the voltage and the current in the circuit. (4)

[20]

**QUESTION 5**

- 5.1 The value of a resistor is measured by the voltmeter-ammeter method. The internal resistance of the voltmeter is  $800 \Omega$ . When the voltmeter is connected directly across the resistor to be measured, the ammeter reads 1,25 A and the voltmeter 200 V.

Calculate the value of the unknown resistor as follows:

- 5.1.1 Approximately (1)
- 5.1.2 Accurately (3)
- 5.1.3 The percentage error in the value of the resistor (2)
- 5.2 The no-load current of a 3 000/150-V single-phase transformer is 25 A at a power factor of 0,3. The primary winding has 150 turns and the supply frequency is 60 Hz.
- Calculate the following:
- 5.2.1 The maximum value of the flux in the core
- 5.2.2 The power loss on no-load
- 5.2.3 The value of the magnetising current (2 x 3) (6)
- 5.3 Name THREE types of power stations used to generate electricity. (3)
- 5.4 Why is the rotor bars of an induction motor skewed? (2)
- 5.5 Name the THREE main parts of an induction motor. (3)

**[20]****TOTAL: 100**

# ELECTROTECHNICS N4

## FORMULA SHEET

Any applicable formula may also be used.

### 1. Principles of electricity

$$E = V + Ir$$

$$V = IR$$

$$R_{se} = R_1 + R_2 + \dots R_n$$

$$R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots \frac{1}{R_n}}$$

$$R = \rho \frac{\ell}{a}$$

$$\frac{R_1}{R_2} = \frac{1 + \alpha_o T_1}{1 + \alpha_o T_2}$$

$$R_t = R_\theta [1 + \alpha_\theta (t - \theta)]$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$\Phi = \frac{mmf}{S} = \frac{IN}{S}$$

$$H = \frac{IN}{\ell}$$

$$F = B\ell I$$

$$E = \frac{\Delta\Phi}{\Delta t} \cdot N$$

$$E = B\ell v$$

$$E = \frac{L\Delta I}{\Delta t}$$

$$L = \frac{\Delta\Phi}{\Delta I} \cdot N$$

$$Q = VC$$

$$Q_{se} = Q_t = Q_1 = Q_2 \dots = Q_n$$

$$C_{se} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots \frac{1}{C_n}}$$

$$Q_p = Q_1 + Q_2 + \dots Q_n$$

$$C_p = C_1 + C_2 + \dots C_n$$

### 2. Direct-current motors

$$E = \frac{2Z}{c} \cdot \frac{Np}{60} \cdot \Phi$$

$$c = 2a$$

$$E_{gen} = V + I_a R_a$$

$$E_{mot} = V - I_a R_a$$

$$R_{start} = \frac{(V - E)}{I_a} - R_a$$

### 3. Alternating-current motors

$$E_m = 2\pi BANn$$

$$e = E_m \sin (2\pi f \cdot t \times 57,3)^\circ$$

$$E_{ave} = 0,637 E_m$$

$$E_{rms} = 0,707 E_m$$

$$T = \frac{1}{f}$$

$$f = \frac{Np}{60}$$

$$\omega = 2\pi f$$

$$Z_L = R + j\omega L$$

$$Z_C = R - j \frac{1}{\omega C}$$

$$pf = \cos \phi = \frac{R}{Z}$$

$$S = VI$$

$$P = V \cdot I \cos \phi = I^2 R$$

$$Q = V \cdot I \sin \phi$$

#### 4. Transformers

$$E = 4,44 f \Phi_m N$$


$$k_t = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

#### 5. Measuring instruments

$$R_{SH} = \frac{i_m R_m}{I_{sh}}$$

$$R_{se} = \frac{V}{i_m} - R_m$$



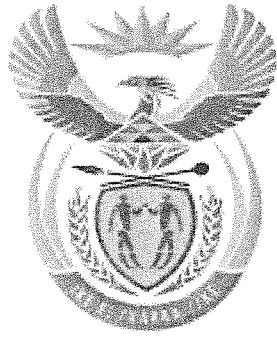

# higher education & training

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

## **MARKING GUIDELINE**

**NATIONAL CERTIFICATE**

**APRIL EXAMINATION**

**ELECTROTECHNICS N4**

**13 APRIL 2015**

**This marking guideline consists of 7 pages.**

## QUESTION 1

1.1  $R_t = R_{20}[1 + \alpha_\theta(t - \theta)]$   
 $= 300[1 + 0,004(200 - 75^\circ)]$   
 $= 300[1 + 0,004(125^\circ)]$   
 $= 300(1,5)$   
 $= 450 \Omega$  (4)

- 1.2
- Positive temperature coefficient of resistance refers to materials whose resistance rises when the temperature increases. ✓
  - Negative temperature coefficient of resistance refers to materials whose resistance falls when the temperature increases. ✓
- (3)

1.3 1.3.1  $L = 1\,500 \times 0,4 = 600 \text{ m } \checkmark$

$$R = \frac{\rho \times L}{A} \checkmark \checkmark$$

$$= \frac{4 \times 10^{-6} \times 600}{300 \times 10^{-6}} \checkmark \checkmark$$

$$= 8 \Omega$$

(5)

1.3.2  $E = \frac{LI}{t} \times 2 \checkmark$   
 $= \frac{3 \times 60}{15} \times 2$   
 $= 24 \text{ V } \checkmark$  (2)


1.4 1.4.1  $C = Q/V = 400/40 \quad \& = 400/10$   
 $= 10 \mu\text{F } \checkmark \checkmark \quad \& = 40 \mu\text{F } \checkmark \checkmark$  (2)

1.4.2  $C_s = \frac{1}{\frac{1}{10} + \frac{1}{40}} = 8 \mu\text{F } \checkmark \checkmark$  (4)  
**[20]**

**QUESTION 2**

2.1 The sum of the currents flowing towards a junction is equal to the sum of the currents flowing away from that junction  $\checkmark\checkmark$  (2)

2.2

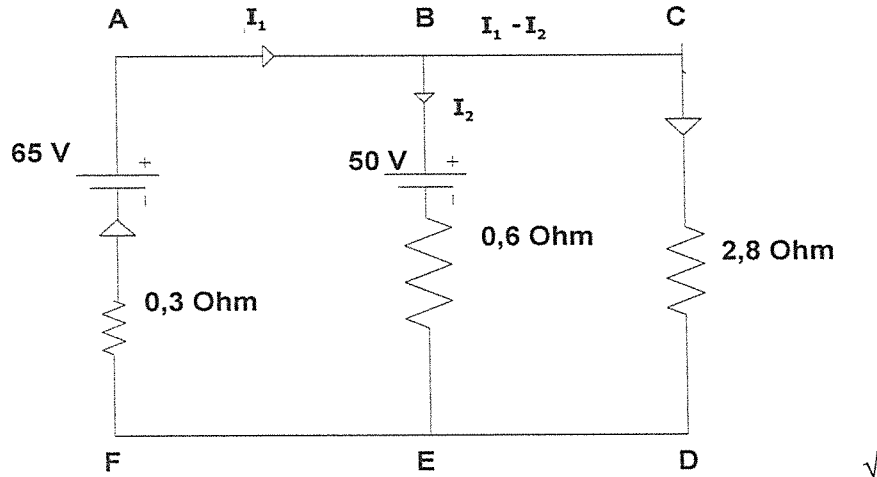

2.2.1 Consider loop/Vanaf lus: ABEFA :loop/lus: ACDF A  
 $\sum E - \sum IR = 0$   $\sum E - \sum IR = 0$   
 $(E_1 - E_2) - (I_1 R_1 + I_2 R_2) = 0$   $(E_1 - (I_1 R_1 + R_3(I_1 - I_2))) = 0$   
 $(65 - 50) - (0,3I_1 + 0,6I_2) = 0 \checkmark$   $65 - (0,3I_1 + 2,8I_1 - 2,8I_2) = 0$   
 $15 - 0,3I_1 - 0,6I_2 = 0 \dots\dots\dots(1)$   $65 - 3,1I_1 + 2,8I_2 = 0 \dots\dots$   
 Eq./Verg. (1) x 4,667 =  $70 - 1,4I_1 - 2,8I_2 = 0$   
 .....(3)  $\checkmark$   
 Eq./Verg. (2) + (3) =  $\underline{135 - 4,5I_1 = 0 \checkmark}$   
 Thus/Dus:  $I_1 = 135/4,5 = \underline{30 A}$   
 Substitute/Vervang  $I_1 = 30 A$  into/in Eq./Verg. (1)  
 $15 - 0,3(30) = 0,6I_2$   
 $I_2 = 15 - 9 / 0,6 = - 6/0,6 = \underline{10 A}$   
 $I_1 - I_2 = 30 - 10 = \underline{20 A} \checkmark$

Current across 65-V Battery = 30 A  $\checkmark$

Current across 50-V Battery = 10 A  $\checkmark$  (7)

2.2.2 Voltage across the load =  $IR = 20 \times 2,8 = \underline{56 V} \checkmark$  (2)

2.3 One farad is that capacitance which will accumulate a charge of 1 coulomb when connected across a voltage of 1 volt  $\checkmark\checkmark\checkmark$  (3)

2.4 2.4.1  $V_{SE} = IR_{SE} = 4 \times 25 = \underline{100 V} \checkmark$

$R_p = \frac{V_p}{I_T} = \frac{180}{4} = 45 \Omega \checkmark$

$V_T = V_{SE} + V_p$

$280 = 100 + V_p$

$V_p = \underline{180 V} \checkmark$

$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R} \quad \frac{1}{R_x} = \frac{1}{R_p} - \frac{1}{R_1} \quad \checkmark = \frac{1}{45} - \frac{1}{180}$


$\frac{1}{R_x} = 0,0167 \quad \therefore \quad R_x = \underline{60 \Omega} \checkmark$  (5)

2.4.2  $P = VI = 280 \times 4 = \underline{1120 W} \checkmark$  (1)

[20]

QUESTION 3

3.1

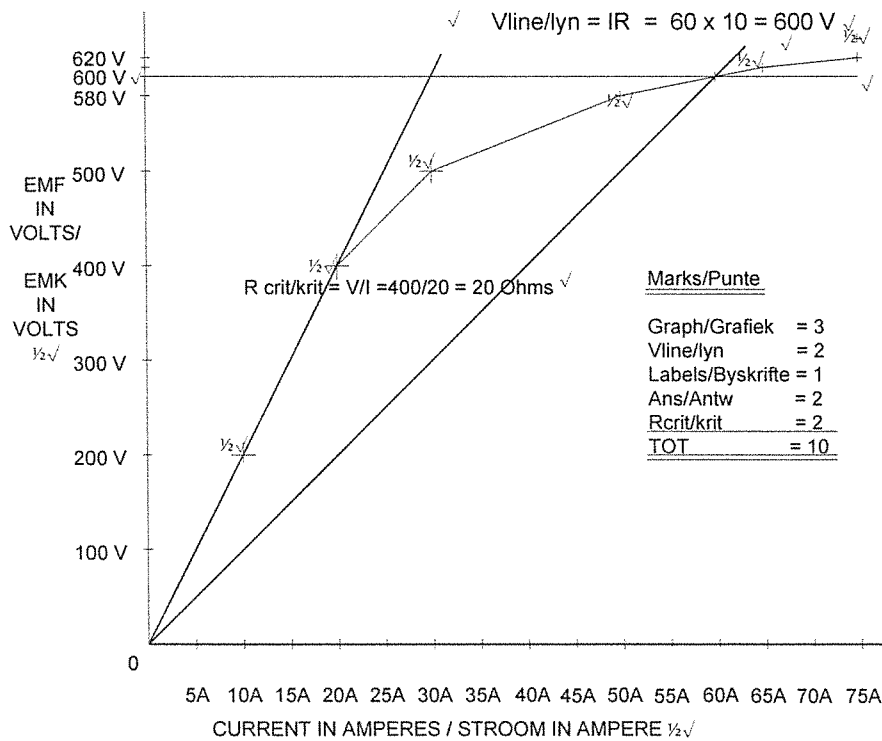

(10)

3.2

$I_{SH} = \frac{V}{R_{SH}} = \frac{480}{48} \checkmark = 10 A$

$I_a = I_L - I_{SH} = 210 - 10 \checkmark = 200 A$

$E = V - I_a R_a + I_a R_{SE} = 480 - [(200 \times 0,3) + (200 \times 0,1)] \checkmark \checkmark \checkmark$

$= 480 - (60 + 20)$

$= \underline{400 V}$  (5)

- 3.3 To hold the field windings in place and to increase the cross-sectional area  $\checkmark\checkmark$  (2)
- 3.4
- Air $\checkmark$
  - Paper $\checkmark$
  - Mica $\checkmark$
  - Ceramic
  - Polycarbonate
  - Electrolytic
- (Any 3 x 1) (3)  
[20]

**QUESTION 4**

- 4.1 Making the circuit more capacitive  $\checkmark$  To run a synchronous motor with little or no load with rotor over-excited by a high direct current $\checkmark$  By use of suitable corrective apparatus (machines)  $\checkmark$  (Any 2 x 1) (2)

4.2 4.2.1  $V_{rms}/\omega k = 0,707V_m$   
 $424,2 = 0.707V_m \checkmark$   
 $V_m = \frac{424,2}{0,707}$   
 $= 600 \text{ V}$

$$v = V_m \sin 2\pi f t \times \frac{180}{\pi}$$


$$300 = 600 \sin 2\pi 50 t \frac{180}{\pi} \checkmark\checkmark\checkmark\checkmark$$

$$\frac{250}{500} = \sin 18\,000 t$$

$$1\,8000t = \sin^{-1} 0,5$$

$$t = \frac{30}{1\,8000} = 1,67 \text{ ms} \quad (4)$$


4.2.2

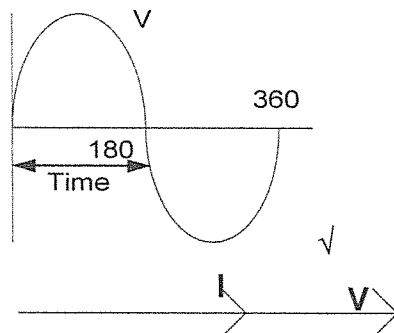

(2)

4.3 4.3.1  $X_L = 2\pi fL = 2\pi 50 \times 0,3183 = 100 \Omega \checkmark$   
 $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi 50 \times 1,061 \times 10^{-6}} = 300 \Omega \checkmark$   
 $Z_{COIL} = \sqrt{R^2 + X_L^2} = \sqrt{200^2 + 100^2} = 223,607 \Omega \checkmark$   
 $Z = \sqrt{R^2 + (X_C^2 - X_L^2)} = \sqrt{200^2 + (300 - 100)^2} = 282,843 \Omega \checkmark$   
 $I = V/Z = 565,685/282,843 = 2 \text{ A} \checkmark$   
 $\Theta = \text{Cos}^{-1} \frac{R}{Z} = \text{Cos}^{-1} \frac{200}{282,843} = 45^\circ \checkmark$   
 $V_{COIL} = IZ_{COIL} = 2 \times 223,607 = 447,214 \text{ V} \checkmark$  (7)

4.3.2  $V_C = IX_C = 2 \times 300 = 600 \text{ V} \checkmark$  (1)

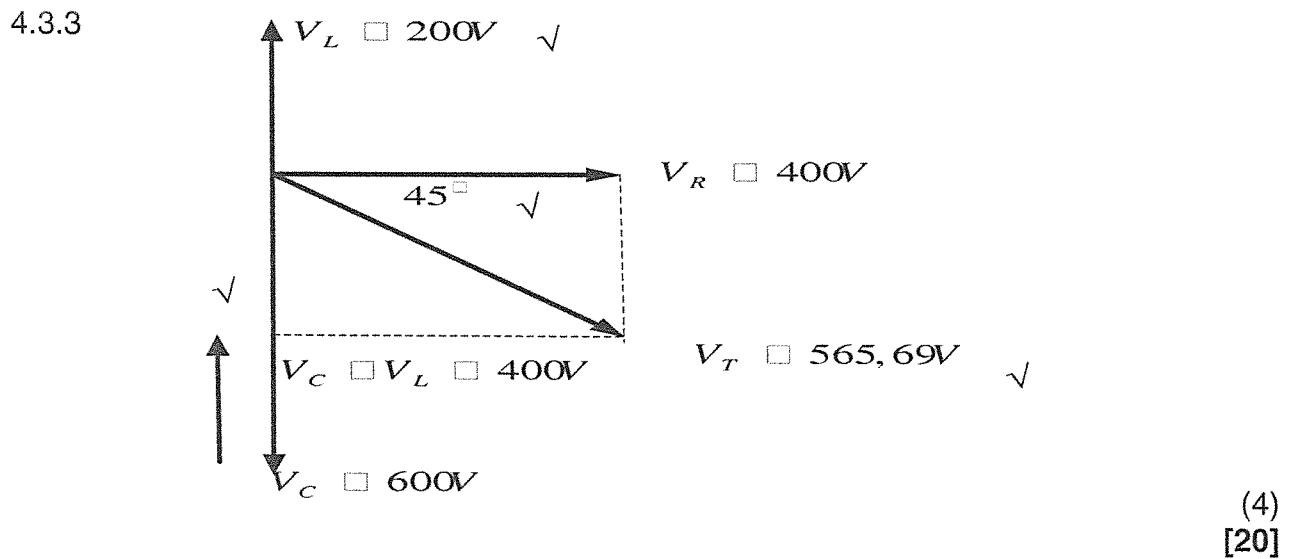

QUESTION 5

5.1 5.1.1  $R_V = 800\Omega \quad V = 200 \text{ V} \quad I = 1,25 \text{ A}$   
 $R_{app} = \frac{V}{I} = \frac{200}{1,25} = 160A \checkmark$   
 $I_V = \frac{V}{R_V} = \frac{200}{800} = 0,25A \checkmark$  (1)

5.1.2  $R_X = \frac{V}{I - I_V} = \frac{200}{1,25 - 0,25} = 200\Omega \checkmark \checkmark$  (3)

5.1.3  $\% \text{ Error} = \frac{R_X - R_{app}}{R_X} = \frac{200 - 160}{200} = 20\% \checkmark \checkmark$  (2)

- 5.2      5.2.1       $E_1 = 4,44\Phi_m fN_1$   
 $\Phi_m = E_1 / 4,44fN_1 = 3\,000 / 4,44 \times 60 \times 150 = 0,075075 = 75,075$   
mWb√√
- 5.2.2       $Powerloss = V_1 I_0 \cos\phi_0 = 3000 \times 25 \times 0,3 = 22,5Kw \checkmark\checkmark$
- 5.2.3       $I_C = \frac{Coreloss}{V_P} = \frac{22500}{3000} = 7,5A \checkmark$   
 $I_M = \sqrt{I_o^2 - I_C^2} = \sqrt{25^2 - 7,5^2} = 23,484A \checkmark$
- (3 x 2)      (6)
- 5.3      • Coal-fired power station  
• Hydro-electric power station  
• Nuclear power station
- (3)
- 5.4      To reduce magnetic noise and to eliminate variation in starting torque at different positions of the rotor √√
- (2)
- 5.5      • Rotor  
• Stator  
• End plates
- (3)  
[20]
- TOTAL:      100**