



**higher education
& training**

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE

NATIONAL CERTIFICATE

APRIL EXAMINATION

ELECTROTECHNICS N4

12 APRIL 2016

This marking guideline consists of 8 pages.

QUESTION 1

1.1 1.1.1 $C_s = \frac{1}{\frac{1}{12} + \frac{1}{6}} = 4 \mu F \checkmark \checkmark \checkmark$ (2)

1.1.2 $Q_T = Q_1 = Q_2 = VC = 20 \times 4 \mu F = 80 \mu C \checkmark \checkmark$
 $V = Q/C = 80/12 \text{ \& } 80/6$
 $= 6,67 V \checkmark \text{ \& } 13,33 V \checkmark$ (4)

1.2 Eddy currents \checkmark They heat up the core \checkmark and is a waste of energy \checkmark (3)


1.3 1.3.1 $I_a = I_T - I_c$
 $= 300 - 100 \checkmark$
 $= 200 A$
 $A_a = \frac{\pi d_a^2}{4} = \frac{\pi (5 \times 10^{-3})^2}{4} = 1,963495408 \times 10^{-5} m^2 \checkmark \checkmark$
 $R_a = \frac{P_a \times L_a}{A_a}$ but
 $= \frac{0,028 \times 10^{-6} \times 1500}{1,963495408 \times 10^{-5}} \checkmark$
 $= 2,139042435 \Omega$ (4)

1.3.2 $\checkmark d = \sqrt{\frac{4P_c L_c}{\pi R_c}} = \sqrt{\frac{4 \times 0,018 \times 10^{-6} \times 1500}{\pi (4,27808487)}} = 2,835 \text{ mm} \checkmark$
 $V_a = I_a R_a$
 $= 200 \times 2,139042435 = 427,808487 V \checkmark$
 $R_c = \frac{V_c}{I_c} = \frac{427,8084870}{100} = 4,27808487 \Omega \checkmark$ (4)

1.4 $R_t = R_{30} [1 + \alpha_{30} (t - 40^\circ)]$
 $= 500 [1 + 0,004 (60^\circ - 40^\circ)]$
 $= 500 [1 + 0,004 (20)] \checkmark \checkmark \checkmark$
 $= 540 \Omega$
 $= 540 - 500 = 40 \Omega$ (3)
[20]

QUESTION 2

2.1

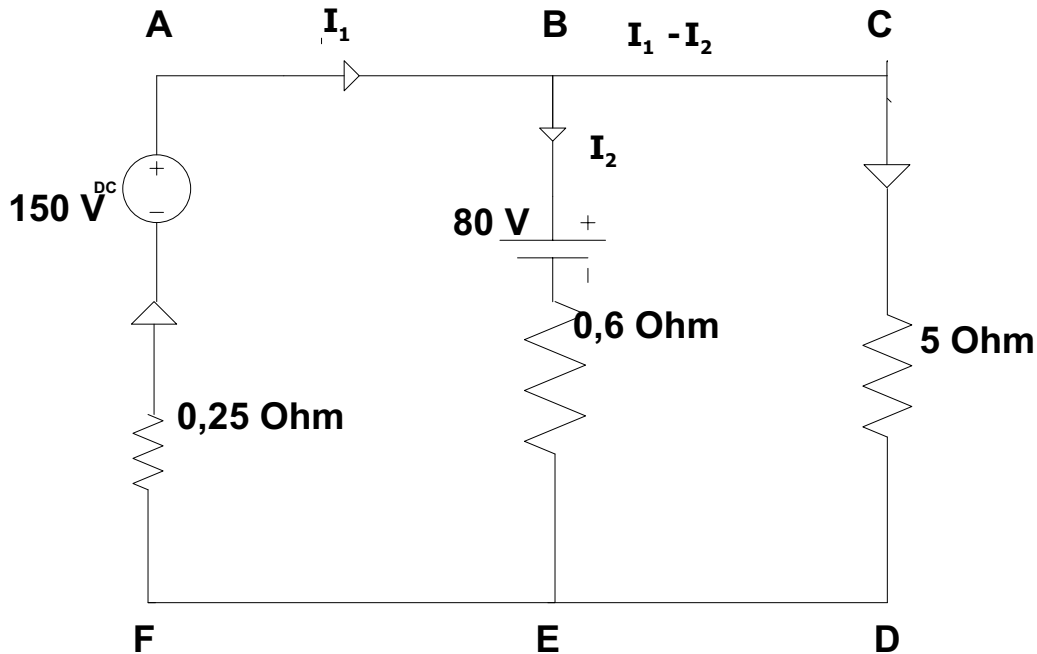

Consider loop: ABEFA
 $\sum E - \sum IR = 0$
 $(E_1 - E_2) - (I_1 R_1 - I_2 R_2) = 0$

:loop:ACDFA
 $\sum E - \sum IR = 0$

$$(E_1 - E_2) - (I_1 R_1 - I_2 R_2) = 0$$

$$(150 - 80) - (0,25 I_1 - 0,6 I_2) = 0 \checkmark$$

$$70 - 0,25 I_1 + 0,6 I_2 = 0 \dots\dots\dots(1)$$

$$E - [I_1 R_1 + R_3 (I_1 - I_2)] = 0$$

$$150 - 0,25 I_1 - 5 I_1 + 5 I_2 = 0 \checkmark$$

$$150 - 5,25 I_1 + 5 I_2 = \dots\dots\dots(2)$$

Eq. (1) x (5/0,6) = $\underline{583,333 - 2,0833 I_1 + 5 I_2 = 0} \checkmark \dots(3)$

Add (2) and (3) = $733,333 - 7,333 I_1 = 0$

Thus: $I_1 = 733,333 / 7,333 = \underline{100 A} \checkmark$

Substitute $I_1 = 100 A$ into Eq. (1)

$$70 - 0,25(100) + 0,6 I_2 = 0$$

$$-I_2 = 70 - 25 / 0,6 = -45 / 0,6$$

$$-I_2 = -\underline{75 A} \text{ Thus} \checkmark$$

$$I_2 = \underline{75 A}$$

$$I_1 - I_2 = 100 - 75 = 25 A$$

2.1.1 $I_1 = 100 A$ from pos. to neg. \checkmark (5)

2.1.2 $I_2 = 75 A$ from neg. to pos. \checkmark (2)

2.1.3 $V_L = 25 \times 5 = 125 V. \checkmark$ (2)

$$\begin{aligned}
 2.2 \quad V &= I R \\
 100 &= 20 R \\
 R_T &= \underline{5 \Omega} \checkmark
 \end{aligned}$$

$$\begin{aligned}
 2.2.1 \quad R_{SE} = R_T - R_P &= 5 - \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} & \therefore V_{SE} = I R_{SE} & V_P = V_T - V_{SE} \\
 &= 5 - \frac{1}{\frac{1}{9} + \frac{1}{9}} \checkmark & = 20 \times 0,5 & = 100 - 10 \\
 &= 5 - \frac{1}{0,222} & = \underline{10V} \checkmark & = \underline{90V} \checkmark \\
 &= 5 - 4,5 \\
 &= \underline{0,5 \Omega} \checkmark & &
 \end{aligned} \tag{5}$$

$$2.2.2 \quad I_p = \mathbf{20A}$$

$$\text{but } V_p = \mathbf{90V}$$


$$\begin{aligned}
 \therefore I_{5\Omega} &= \frac{V_p}{R_1} = \frac{90}{9} = \mathbf{10A} \checkmark \checkmark \\
 I_{20\Omega} &= \frac{V_p}{R_2} = \frac{90}{9} = \mathbf{10A} \tag{2}
 \end{aligned}$$

2.3 Ampere is defined as the current which is maintained in two straight parallel conductors of infinite length of negligible cross-sectional area, and placed 1 metre apart in a vacuum, would produce between the conductors a force of 2×10^{-7} Newton per metre of length. $\checkmark \checkmark \checkmark$ (3)

2.4 They are almost unaffected by temperature \checkmark (1)
[20]

QUESTION 3

3.1

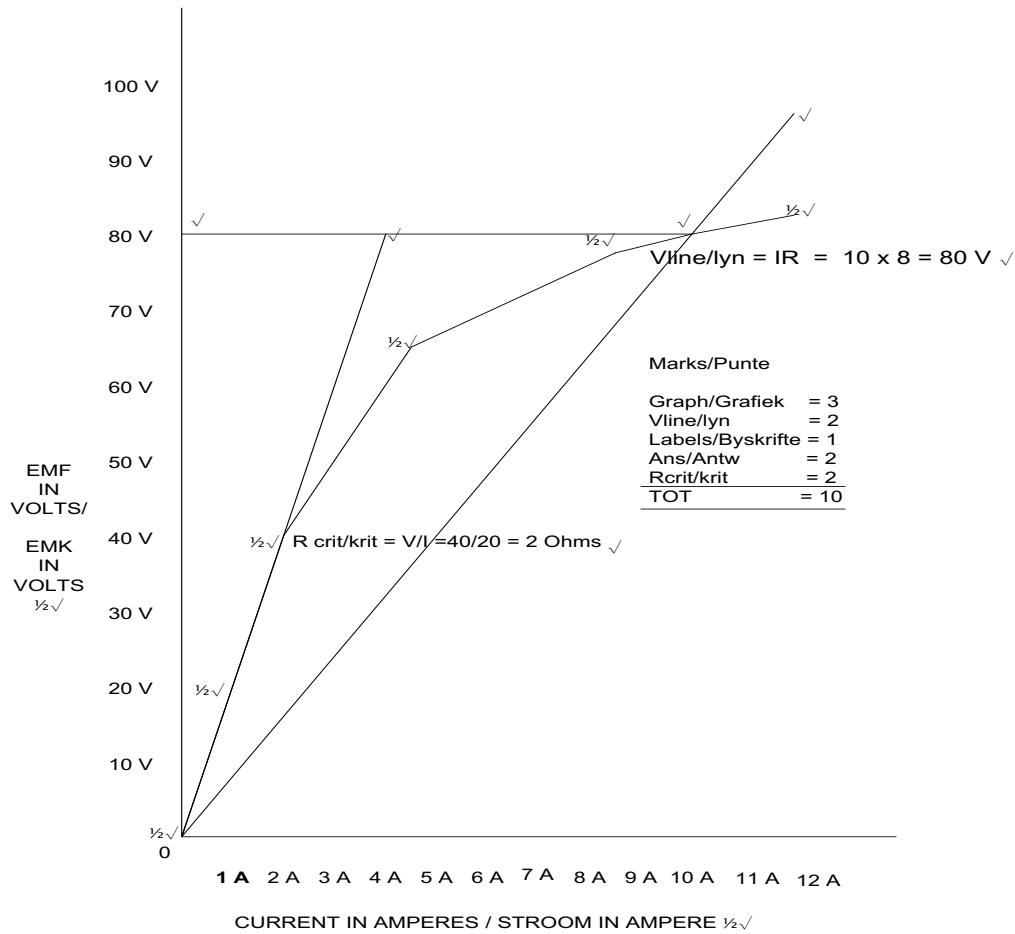

(10)

3.2

$$I_{SH} = \frac{V + I_L R_{SE}}{R_{SH}}$$

$$= \frac{290 + (40 \times 0,25)}{30}$$

$$= \frac{300}{30}$$

$$= 10 \text{ A}$$

$$I_a = I_L + I_{SH}$$

$$= 40 + 10$$

$$= 50 \text{ A}$$

$$E = V + I_a R_a + I_L R_{SE}$$

$$= 290 + (50 \times 0,4) + (40 \times 0,25)$$

$$= 320 \text{ V}$$

(5)

- 3.3
- Brush shifting ✓
 - Using interpoles ✓
 - By placing compensating windings in the pole shoes ✓
- (3)

- 3.4 To limit the initial starting current to an acceptable value ✓✓
- (2)
[20]

QUESTION 4

4.1 $E_1 = 4,44 \Phi_m f N_1$

4.1.1 $\Phi_m = E_1 / 4,44 f N_1$
 $= 1110 / 4,44 \times 50 \times 200 \times 10 \times 10^{-4}$
 $= \underline{25 \text{ Tesla}} \check{\check{\check{}}}$

(3)

4.1.2 $N_2 = \frac{V_2 \times N_1}{V_1} = \frac{111 \times 200}{1110} = \underline{20 \text{ Turns}} \check{\check{}}$

(2)

4.2 4.2.1 $V_{\text{rms}} = 0,707 V_m$
 $V_m = \frac{424,2}{0,707} = 600 \text{ V} \check{}$

4.2.2 $T = \frac{1}{f}$
 $f = \frac{1}{t} = \frac{1}{25 \times 10^{-3}} = \underline{40 \text{ Hz}} \check{}$

(2 x 1) (2)

4.3 $i_1 = 6,708 - 30 \angle \infty = 5,8093 + j3,354$
 $i_2 = 6,708 - - 30 \angle \infty = 5,8093 - j3,354 \check{\check{}}$

Total current $= 11,6186 + j 0$
 $= 11,6186 \angle 0^\circ \check{}$

$i_T = \underline{11,6186 \text{ Sin}(wt + 0 \angle \infty) \text{ A}} \check{}$

(4)

- 4.4 4.4.1 $\mathbf{Z}_1 = 15 + j10 = 18,03 - 33,69^\circ \checkmark$
 $\mathbf{Z}_2 = 15 - j10 = 18,03 - - 33,69^\circ \checkmark$
 $\mathbf{Z}_1 + \mathbf{Z}_2 = 30 - j0 = 30 \angle 0^\circ \Omega \checkmark$

$$\mathbf{Z}_T = \frac{\mathbf{Z}_1 \times \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$

$$= \frac{18,03 - 33,69^\circ \times 18,03 - - 33,69^\circ \checkmark}{30 - 0^\circ}$$

$$= 10,833 - 0^\circ = 10,833 - j0, \Omega$$
- $V = I Z \therefore \mathbf{I}_T = \frac{V}{Z_T} = \frac{270,825 - 0^\circ}{10,833 - 0^\circ} = 25 \angle 0^\circ \text{A} \checkmark$ (4)
- 4.4.2 $\mathbf{I}_1 = \frac{V}{Z_1} = 270,825 - 0^\circ / 18,03 - 33,69^\circ = 15,023 - - 33,69^\circ \text{A} \checkmark$ (1)
- 4.4.3 $\mathbf{I}_1 = \frac{V}{Z_1} = 270,825 - 0^\circ / 18,03 - 33,69^\circ = 15,023 - - 33,69^\circ \text{A} \checkmark$
 $\mathbf{I}_2 = \frac{V}{Z_2} = 270,825 - 0^\circ / 18,03 - 33,69^\circ = 15,023 - 33,69^\circ \text{A} \checkmark$ (2)
- 4.4.4 $P = V^2/R = 270,825^2/10,833 = 6,77 \text{ Kw}$ or
 $P = I^2R = 25^2 \times 10,833 = 6,77 \text{ kW}$ or
 $P = VI = 270,825 \times 25 = 6,77 \text{Kw} \checkmark$ (1)
- 4.4.5 $\text{Cos}\theta = \frac{R}{Z} = \frac{10,833}{10,833} = 1 \checkmark$ (1)
[20]

QUESTION 5

- 5.1 5.1.1 $\frac{V_p}{V_s} = \frac{N_p}{N_s} \therefore V_p = \frac{V_s N_p}{N_s} = \frac{200 \times 40}{20} = 400 \text{ V} \checkmark \checkmark$ (2)
- 5.1.2 $\therefore I_p = \frac{V_s I_s}{V_p} = \frac{200 \times 20}{400} = 10 \text{ A} \checkmark \checkmark$ (2)
- 5.1.3 $P = V_s I_s \text{Cos } Q = 200 \times 20 \times 0,6 = 2400 \text{ W} \checkmark$ (1)
- 5.2 Air, Paper, Mica, Ceramic, Polycarbonate, Electrolytic (Any 3 x 1) (3)

- 5.3 It produces a constant torque and lets the motor run quietly and ensures that it operates at a good power factor. ✓✓✓ (3)
- 5.4 Natural cooling by atmospheric circulation ✓
Oil-immersed with natural cooling ✓ (2)
- 5.5 Radial and ring feeders ✓✓ (2)
- 5.6
$$\mathbf{I_V = \frac{V}{R_V} = \frac{200}{800} = 0,25 \text{ A } \checkmark}$$
$$\mathbf{I_R = \frac{V}{R} = \frac{200}{200} = 1 \text{ A } \checkmark}$$
$$\mathbf{I_T = I_R + I_V = 1 + 0,25 = 1,25 \text{ A } \checkmark}$$
$$\mathbf{V_X = V_T - V_R = 400 - 200 = 200 \text{ V } \checkmark}$$
$$\mathbf{R_x = \frac{V_x}{I_T} = \frac{200}{1,25} = 160 \Omega \checkmark}$$

(5)
[20]**TOTAL: 100**