



**higher education
& training**

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE


**NATIONAL CERTIFICATE
NOVEMBER EXAMINATION
ELECTROTECHNICS N4**

30 NOVEMBER 2016

This marking guideline consists of 7 pages.

QUESTION 1

1.1

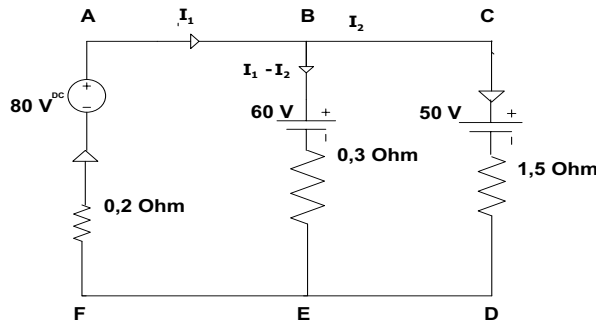

Consider loop: ABEFA

$$\sum E - \sum IR = 0$$

$$(E_1 - E_2) - (I_1 R_1 + (I_1 R_2 - I_2 R_2)) = 0$$

$$(80 - 60) - (0,2 I_1 + (0,3 I_1 - 0,3 I_2)) = 0 \checkmark$$

$$20 - 0,5 I_1 + 0,3 I_2 = 0 \dots\dots\dots(1)$$

$$(E_1 - E_3) - [I_1 R_1 + R_3 I_2] = 0$$

$$(80 - 50) - (0,3 I_1 + 1,5 I_2) = 0 \checkmark$$

$$30 - 0,3 I_1 - 1,5 I_2 = 0 \dots\dots\dots(2)$$

$$\text{Eq./Verg. (1) x (5)} = \underline{100 - 2,5 I_1 + 1,5 I_2 = 0} \checkmark \dots\dots\dots(3)$$

$$\text{Add (2) and (3)} = 130 - 2,8 I_1 = 0$$

$$\text{Thus: } I_1 = 130/2,8 = \underline{46,43 \text{ A}} \checkmark$$

Substitute $I_1 = 10 \text{ A}$ into Eq. (1)

$$20 - 0,5(46,43) + 0,3 I_2 = 0$$

$$-I_2 = 20 - 23,2143/0,3 = -3,2143/0,3$$

$$-I_2 = -\underline{10,7143 \text{ A}} \text{ Thus } \checkmark$$

$$I_2 = \underline{10,7143 \text{ A}}$$

$$I_1 - I_2 = \underline{35,7143 \text{ A}}$$

1.1.1 $I_1 = 46,43 \text{ A}$ from pos. to neg. \checkmark

1.1.2 $I_1 - I_2 = \underline{10,7143 \text{ A}}$ from neg. to pos. \checkmark

1.1.3 $I_2 = 10,7143$ from neg. to pos. \checkmark

(8)

- 1.2 $P = I^2 R$
 $1000 = 100 R$
 $R = \underline{10 \Omega} \checkmark \times$
 $\therefore V_{SE} = IR_{SE} \quad V_P = V_T - V_{SE} \quad I = V/R$
 $\quad = 10 \times 10 \quad = 190 - 100 \quad = 90/15$
 $\quad = \underline{100V} \checkmark \quad = \underline{90V} \checkmark \quad = \underline{6A} \checkmark$
 $I = 10 - 6 = 4 A \checkmark$
 Maar $V_P = 90 V$
 $\therefore R_x = \frac{V_P}{I} = \frac{90}{4} = \underline{22,50 \Omega} \checkmark \checkmark$ (7)
- 1.3 The type of material used, and the heat treatment and the mechanical handling to which the specimen has been subjected. (3)
- 1.4 They are almost unaffected by temperature. (2)
[20]

QUESTION 2

- 2.1 2.1.1 $C_s = 8 + 10 = 18 \mu F \checkmark \checkmark$
- 2.1.2 $Q_T = Q_1 = Q_2 = VC = 20 \times 18 \mu F = \underline{360 \mu C} \checkmark \checkmark$
 $V = Q/C = 360/8 \quad \& \quad 360/10$
 $= 45 V \checkmark \quad \& \quad 36 V \checkmark$ (6)
- 2.2 Air, Paper, Mica, Ceramic, Polycarbonate, Electrolytic (Any 3 × 1) (3)
- 2.3 2.3.1 $I_a = I_T - I_c$
 $= 350 - 150 \checkmark$
 $= 200 A$
 $A_a = \frac{\pi d_a^2}{4} = \frac{\pi (20 \times 10^{-3})^2}{4} = 3,141592654 \times 10^{-4} m^2 \checkmark \checkmark$
 $R_a = \frac{P_a \times L_a}{A_a} \quad \text{but}$
 $= \frac{0,028 \times 10^{-6} \times 500}{3,141592654 \times 10^{-4}} \checkmark$
 $= 0,04456338407 \Omega$
 $d = \sqrt{\frac{4P_c L_c}{\pi R_c}} = \sqrt{\frac{4 \times 0,017 \times 10^{-6} \times 500}{\pi (0,05941784542)}} = 13,496 mm \checkmark \checkmark$ (6)

2.3.2 $V_a = I_a R_a$
 $= 200 \times 0,04456338407 \checkmark$
 $= 8,912676813 \text{ V}$
 $R_c = \frac{V_c}{I_c} = \frac{8,912676813}{150} = 0,05941784542 \Omega \checkmark$


(2)

2.4 $R_t = R [1 + \alpha (t_1 - t_2)]$
 $232 = 200 [1 + \alpha (100^\circ - 60^\circ)] \checkmark \checkmark \checkmark$
 $232 = 200 [1 + \alpha (40)]$
 $\alpha = 0,004 \text{ per degree C}$

(3)
[20]

QUESTION 3

3.1

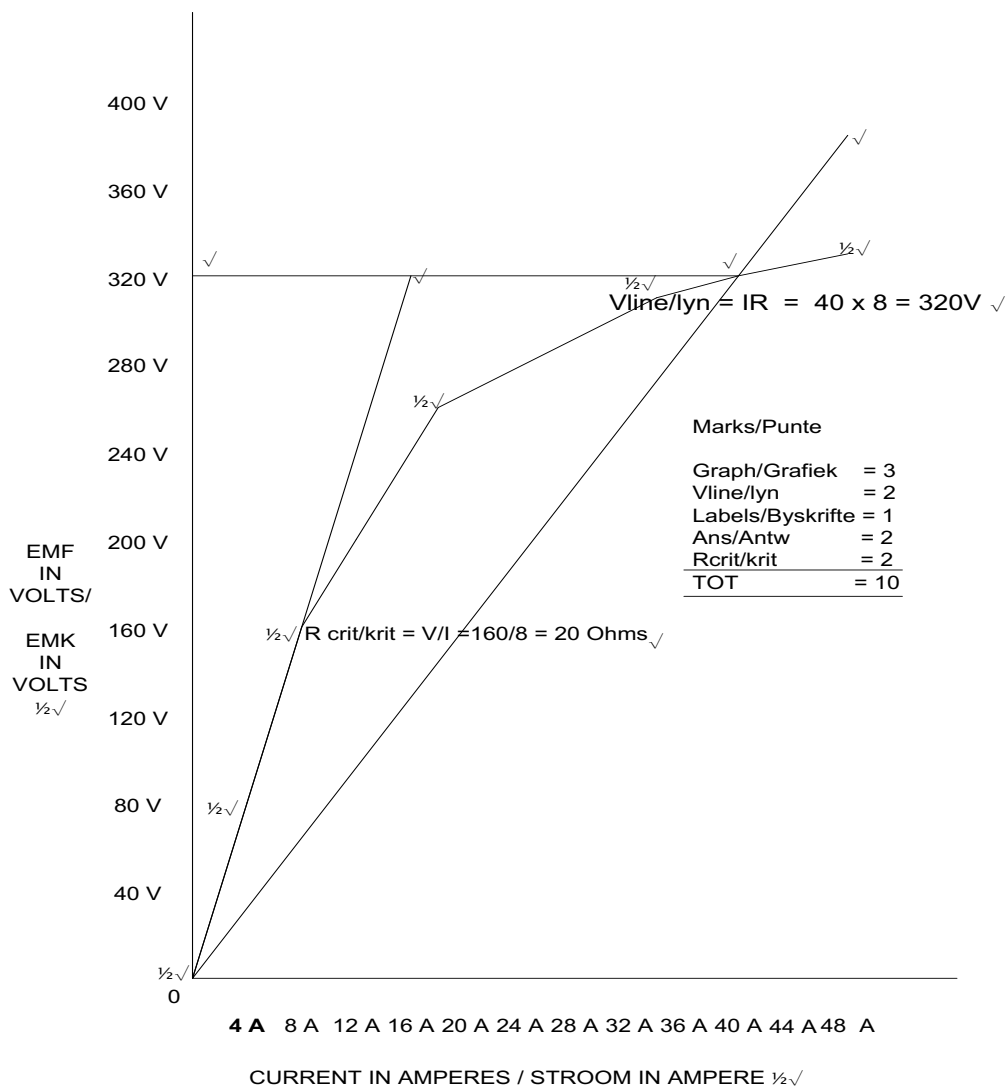

(10)

$$\begin{aligned}
 3.2 \quad I_{SH} &= \frac{V + I_L R_{SE}}{R_{SH}} \\
 &= \frac{360 + (50 \times 0,8)}{10} \quad \checkmark\checkmark \quad I_a = I_L + I_{SH} \quad E = V + I_a R_a + I_L R_{SE} \\
 &= \frac{400}{10} \quad \checkmark\checkmark\checkmark\checkmark \quad = 50 + 40 \quad = 360 + (90 \times 0,2) + 50(0,8) \quad \checkmark\checkmark \\
 &= 40 \text{ A} \quad \checkmark\checkmark \quad = 90 \text{ A} \quad = 418 \text{ V}
 \end{aligned}$$

(5)

3.3 Shunt connected
Series connected
Compound connected

(3)

3.4 To limit the initial starting current to an acceptable value.

(2)
[20]

QUESTION 4

$$\begin{aligned}
 4.1 \quad E_1 &= 4,44 \Phi_m f N_1 \\
 N_1 &= E_1 / 4,44 f \Phi_m \\
 &= 888 / 4,44 \times 50 \times 1 \times 200 \times 10^{-4} \\
 &= \underline{200 \text{ Windings}} \quad \checkmark\checkmark\checkmark\checkmark \\
 N_2 &= \frac{V_2 \times N_1}{V_1} = \frac{888 \text{ 0} \times 100}{444} = \underline{2000 \text{ Windings}} \quad \checkmark\checkmark \\
 V_{rms} &= 0,707 V_m
 \end{aligned}$$

(6)


$$\begin{aligned}
 4.2 \quad 4.2.1 \quad V_m &= 360 / 0,707 = 509,194 \text{ V} \quad \checkmark \\
 4.2.2 \quad T &= \frac{1}{f} \\
 T &= \frac{1}{50} = \underline{20 \text{ ms}} \quad \checkmark
 \end{aligned}$$

(2 × 1) (2)

$$\begin{aligned}
 4.3 \quad 4.3.1 \quad i_1 &= 60 \angle -45^\circ = 42,42641 - j 42,42641 \\
 i_2 &= 30 \angle 30^\circ = 25,98076 + j 15 \quad \checkmark\checkmark \\
 \text{Total current} &= 68,4072 - j 27,426 \quad \checkmark \\
 &= 73,7 \angle -21,8473^\circ \quad \checkmark \\
 i_T &= \underline{73,7 \text{ Sin}(wt - 21,8473^\circ) \text{ A}} \quad \checkmark
 \end{aligned}$$

(5)

4.3.2

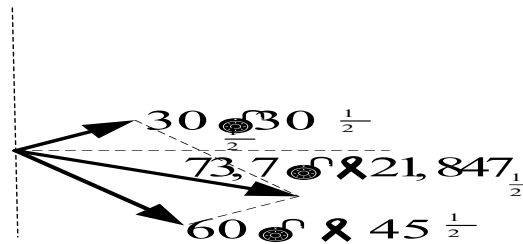

(2)

$$4.4 \quad 4.4.1 \quad \mathbf{Z_1 = 9 + j9 = 12,729 \angle 45^\circ} \quad \mathbf{Z_2 = 3 - j3 = 4,2426 \angle -45^\circ}$$

$$\mathbf{Z_T = 12 + j6 \checkmark}$$

$$\mathbf{Z_T = 13,416 \angle 26,5651^\circ \checkmark}$$

$$\mathbf{V = I Z}$$

(3)

4.4.2

$$\therefore \mathbf{I = \frac{V}{Z}}$$

$$= \frac{\mathbf{268,3282 \angle 0^\circ}}{\mathbf{13,416 \angle 26,5651^\circ}} = 20 \angle -26,5651^\circ = \mathbf{20 A \checkmark \checkmark}$$

$$\text{arbeidsfaktor} = \text{Cos } -26,5651 \text{ lagging} \checkmark$$

$$= 0,894$$

(2)

[20]

QUESTION 5

5.1

$$\mathbf{I_V = \frac{V}{R_V} = \frac{120}{600} = 0,2 A \checkmark}$$

$$\mathbf{I_A = \frac{V}{R_A} = \frac{120}{400} = 0,3 A \checkmark}$$

$$\mathbf{I_T = I_V + I_R = 0,2 + 0,3 = 0,5 A \checkmark}$$

$$\mathbf{V_X = V_T - V_R = 360 - 120 = 240 A \checkmark}$$

$$\mathbf{R_X = \frac{V_X}{I_X} = \frac{240}{0,5} = 480 \Omega \checkmark}$$

(5)

5.2 It serves as a protection system and activates an alarm. (2)

5.3 It produces a constant torque and let the motor run quietly and ensures that it operates at a good power factor. (3)

5.4 Calcium chloride or silica gel which extracts the moisture from the air. (2)

5.5	5.5.1	Radial and ring feeders	(2)
	5.5.2	Radial feeders	(1)
5.6	5.6.1	$\frac{V_p}{V_s} = \frac{N_p}{N_s} \therefore V_s = \frac{V_p N_s}{N_p} = \frac{6\,000 \times 300}{3\,000} = \underline{600\text{ V}} \checkmark$	(1)
	5.6.2	$S = VI \therefore I_s = \frac{S}{V} = \frac{30\,000}{6\,000} = \underline{5\text{ A}} \checkmark$	
		$S = VI \therefore I_p = \frac{S}{V} = \frac{30\,000}{600} = \underline{50\text{ A}} \checkmark$	(2)
	5.6.3	$E = 4,44 \Phi_M f N \therefore \Phi_M = \frac{6\,000}{4,44 \times 60 \times 3\,000} = \underline{7,50571\text{ mWb}}$	$\checkmark \checkmark$
			(2)
			[20]
			TOTAL: 100