



**higher education  
& training**

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

# **MARKING GUIDELINE**

**NATIONAL CERTIFICATE**

**APRIL EXAMINATION**

**ELECTROTECHNICS N5**

**6 APRIL 2016**

**This marking guideline consists of 12 pages.**

**QUESTION 1**

1.1 By reversing either the field✓ or armature connections.✓ (2)

1.2 They are placed in slots in the pole shoes.✓ They are connected in series with the armature windings.✓ (2)

1.3 1.3.1 Ampere turns required on no load =  $6 \times 2\,100 = 12\,600$ ✓  
 Ampere turns required on full load =  $7,5 \times 2\,100 = 15\,750$ ✓  
 Ampere turns required on series field on full load =  $15\,750 - 12\,600$   
 $= 3\,150$ ✓

Full-load line current  $I_L = P/V$   
 $= \frac{355 \times 10^3}{580}$   
 $= 612,07\text{ A}$  ✓  
 Constant field current  $I_f = 6\text{ A}$   
 $I_a = I_L + I_f$   
 $= 618,07\text{ A}$   
 Turns required on series field  $= \frac{3\,150}{618,07}$   
 $= 5,1$  ✓  
 say 6 (5)

1.3.2 With series winding of 12 t/p and resistance of 0,08 Ω

Ampere turns required = 3 150  
 Series field current  $I_f = 3\,150/12$  ✓  
 $= 262,5\text{ A}$  ✓  
 Current through diverter  $R_x = 618,07 - 262,5$   
 $= 355,57\text{ A}$  ✓  
 Voltage across diverter = voltage across series field  
 $(I_x) (R_x)$  =  $I_f (\text{series}) \times R (\text{series})$   
 $R_x = \frac{262,5 \times 0,08}{355,57}$ ✓  
 $= 0,06\ \Omega$ ✓ (5)

1.4  $P = 35 \text{ kW}$   $V = 625$   $p = 2$  ( 4 pole )  $c = 2$  wave-wound  
 $Z = 900$  segments = 150 brush shift = 1,5 segments  
 $I_{sh} = 2,25 \text{ A}$   $\text{Eff} = 85\%$

$$\theta \text{ Mechanical } ^\circ = \frac{1,5}{180} \times 360 ^\circ = 3 ^\circ$$

$$\begin{aligned} \theta \text{ Electrical } ^\circ &= p \times \text{mechanical } ^\circ \\ &= 2 \times 3 ^\circ = 6 ^\circ \checkmark \end{aligned}$$

$$\text{Efficiency} = 85 \% = 0,85$$

$$\text{Input} = \frac{\text{Output}}{\text{Efficiency}} = \frac{35}{0,85} = 41,176 \text{ kW } \checkmark$$

$$I_L = \frac{P \text{ in}}{V} = \frac{41176}{625} = 65,88 \text{ A } \checkmark$$

$$I_a = I_L - I_{sh} = 65,88 - 2,25 = 63,63 \text{ A}$$

$$\begin{aligned} \text{At / p} &= \frac{I Z}{2c2p} \\ &= \frac{(63,63)(900)}{2 \times 2 \times 2 \times 2} \\ &= 3579,18 \quad \checkmark \end{aligned}$$

$$\begin{aligned} \text{Demag At / p} &= \frac{I Z}{2c2p} \times \frac{4\theta}{360} \\ &= 3579,18 \times \frac{4(6)}{360} \\ &= 238,61 \quad \checkmark \end{aligned}$$

$$\begin{aligned} \text{Cross At / p} &= \frac{I Z}{2c2p} \times [1 - \frac{4\theta}{360}] \\ &= 3579,18 [1 - 0,066] \\ &= 3342,95 \checkmark \end{aligned}$$

(6)  
[20]

**QUESTION 2**

$$2.1 \quad 2.1.1 \quad V = 800 \sin ( 314 t + 30 )$$

$$I = 8 \sin ( 314 t + 30 )$$

$$ZT = \frac{800 < 30}{8 < 30} = 100 < 0 \checkmark$$

NATURE

It is a pure resistance because the current is in phase with the voltage. ✓

$$\text{MAGNITUDE : } 100 \text{ ohms} \checkmark \quad (3)$$

2.1.2 Time period (t) of the wave

$$\sin 314 t + 30$$

$$= \sin 2 \pi f t + 30 \quad \checkmark$$

$$2\pi f = 314$$

$$f = 314 / 2 \pi = 49,97 \text{ Hz} \quad \checkmark$$

$$t = 1/49,97 = 20 \text{ ms} \quad \checkmark \quad (3)$$

$$2.2 \quad 2.2.1 \quad fr = \frac{1}{2\pi \sqrt{LC}}$$

$$10^6 = \frac{1}{2\pi \sqrt{140 \times 10^{-6} (C)}}$$

$$\sqrt{140 \times 10^{-6} (C)} = \frac{1}{2\pi 10^6} \checkmark$$

$$140 \times 10^{-6} (C) = \left( \frac{1}{2\pi 10^6} \right)^2$$

$$= 2,533 \times 10^{-14} \checkmark$$

$$C = 1,809 \times 10^{-10}$$

$$= 180,9 \times 10^{-12} \quad 180,9 \text{ pf} \checkmark \quad (3)$$

$$\begin{aligned}
 2.2.2 \quad Z_P &= \frac{L}{CR} = \frac{140 \times 10^{-6}}{180,9 \times 10^{-12} \times 8,25} \\
 &= 93\,807,06 \, \Omega \quad \checkmark \quad (2)
 \end{aligned}$$

$$\begin{aligned}
 2.2.3 \quad R_T &= Z_P + R_{\text{ser}} \\
 &= 93\,807,06 + 7\,300 \\
 &= 101\,107,06 \, \Omega \quad \checkmark
 \end{aligned}$$

$$I_T = \frac{V}{R_T} = \frac{380}{101107,06} = 3,76 \text{ mA} \checkmark$$

$$\begin{aligned}
 V_P &= I_T \times Z_P = 0,00376 \times 93\,807,06 \\
 &= 352,71 \text{ V} \checkmark
 \end{aligned}$$

$$\begin{aligned}
 X_L &= 2\pi f L = X_C \\
 &= 2\pi (10^6) (140 \times 10^{-6}) \checkmark \\
 &= 879,65 \quad \checkmark
 \end{aligned}$$

$$\begin{aligned}
 Z_{\text{coil}} &= \sqrt{R^2 + X_L^2} \\
 &= \sqrt{8,25^2 + (879,65)^2} \\
 &= 879,69 \checkmark
 \end{aligned}$$

$$\begin{aligned}
 I_{\text{coil}} &= \frac{V_P}{Z_{\text{coil}}} \\
 &= \frac{352,71}{879,69} \\
 &= 400,95 \text{ mA} \quad \checkmark
 \end{aligned}$$

$$I_L = 400,95 \text{ mA} \quad \checkmark = I_C$$

**OR**

$$\begin{aligned}
 I_C &= \frac{V_P}{X_C} \\
 &= \frac{352,71}{879,65} \\
 &= 400,96 \text{ mA} \quad \checkmark
 \end{aligned}$$

(9)  
[20]

**QUESTION 3**

- 3.1 Making the transformer window long and narrow. ✓  
 Arranging primary and secondary windings concentrically. ✓  
 Sandwiching primary and secondary windings. ✓  
 Using shell-type construction. ✓

(Any 3 × 1) (3)

- 3.2 Single-phase transformer

24 kVA          3200 /800

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{3200}{800} = 4$$

$$R_1 = 8,4 \quad x_1 = 14,4$$

$$R_2 = 0,75 \quad x_2 = 1,5$$

$$\cos \Phi = 0,8 \quad \Phi = 36,87$$

$$R_e = R_1 + R_2 (N_1/N_2)^2$$

$$= 8,4 + 0,75 (4)^2$$

$$= 20,4 \checkmark$$

$$X_e = X_1 + X_2 (N_1/N_2)^2$$

$$= 14,4 + 1,5 (4)^2$$

$$= 38,4 \quad \checkmark$$

$$Z_e = R_e + j X_e$$

$$= 20,4 + j 38,4$$

$$= 43,48 \angle 62 \quad \checkmark$$

$$VA = I_1 \times 3200 \quad I_1 = \frac{24000}{3200} = 7,5 \text{ A}$$

$$\begin{aligned} \text{Reg} &= \frac{I_1 (\text{Re} \cos \Phi + X_e \sin \Phi)}{V_1} \\ &= \frac{7,5 [20,4 (0,8) + 38,4 (0,6)]}{3200} \quad \checkmark \\ &= 0,092 \text{ p.u.} \\ &= 9,2 \% \quad \checkmark \end{aligned}$$

$$\begin{aligned} V_d &= 800 \times 0,092 \\ &= 73,6 \text{ V} \quad \checkmark \end{aligned}$$

$$\begin{aligned} \text{Full load } V_2 &= \text{No load } V_2 - \text{voltage drop} \\ &= 800 - 73,6 \\ &= 726,4 \text{ V} \quad \checkmark \end{aligned}$$

(7)

$$\begin{aligned} 3.3 \quad 3.3.1 \quad X_L &= 2 \pi f L \\ &= 2 \pi \times 50 \times 0,038 \\ &= 11,94 \quad \checkmark \\ Z_1 = Z_2 = Z_3 &= 29 + j 11,94 \\ &= 31,36 \angle 22,378^\circ \quad \checkmark \\ V_L = V_p &= 535 \text{ V} \\ I_p &= \frac{V_p}{Z_1} = \frac{535 \angle 0^\circ}{31,36 \angle 22,378^\circ} \quad \checkmark \\ &= 17,06 \angle -22,378^\circ \quad \checkmark \end{aligned}$$

$$\begin{aligned} I_L &= \sqrt{3} I_p \\ &= \sqrt{3} \times 17,06 \quad \checkmark \\ &= 29,55 \text{ A} \quad \checkmark \end{aligned} \quad (6)$$

$$3.3.2 \quad \text{Pf} = \cos \Phi = \cos 22,378^\circ \checkmark = 0,925 \text{ lagging} \quad \checkmark \quad (2)$$

$$\begin{aligned} 3.3.3 \quad P &= \sqrt{3} V_L I_L \cos \Phi \\ &= \sqrt{3} \times 535 \times 29,55 \times 0,925 \quad \checkmark \\ &= 25\,329 \text{ kW} \quad \checkmark \end{aligned}$$

(2)  
[20]

**QUESTION 4**

- 4.1 4.1.1  $P_T = \sqrt{3} V_L I_L \cos \phi$
- $$I_L = \frac{135000}{\sqrt{3} \times 2950 \times 0,85}$$
- $$= 31,08 \text{ A} \checkmark$$
- $$I_P = \frac{I_L}{\sqrt{3}} = \frac{31,08}{\sqrt{3}} = 17,94 \text{ A} \checkmark \quad (2)$$
- 4.1.2  $W_1 = V_L I_L \cos (30 + \phi) \quad \phi = 31,79$
- $$= 2950 \times 31,08 \cos (30 + 31,79) \checkmark$$
- $$= 2950 \times 31,08 \cos (61,79)$$
- $$= 43,34 \text{ kW} \checkmark$$
- $$W_2 = V_L I_L \cos (30 - \phi)$$
- $$= 2950 \times 31,08 \cos (30 - 31,79) \checkmark$$
- $$= 91,64 \text{ kW} \checkmark \quad (4)$$
- 4.1.3  $kVA = \frac{\sqrt{3} V_L I_L}{1000}$
- $$= \frac{\sqrt{3} \times 2950 \times 31,08 \text{ A} \checkmark}{1000}$$
- $$= 158,8 \text{ kW} \checkmark \quad (2)$$



4.2      4.2.1      Load  $P = 1,73 \text{ MW} = \frac{1,73\text{MW}}{3}$  per phase

$$\text{COS } \phi = 0,75 \text{ lagging ( sin } \phi = 0,66 )$$

$$V_r = \frac{35000}{\sqrt{3}} (\cos \phi + j \sin \phi)$$

$$= \frac{35000}{\sqrt{3}} (0,75 + j 0,66)$$

$$= 15\,155,44 + j 13\,336,79 \checkmark$$

$$I_p = \frac{1,73 \times 10^6}{\sqrt{3} \cdot 35000 \cdot 0,75} = 38,05 \text{ A} \checkmark$$

$$V_d = I Z = 38,05 (85 + j 155)$$

$$= 3\,234,25 + j 5\,897,75 \checkmark$$

$$V_s = V_r + V_d$$

$$= 15\,155,44 + j 13\,336,79 + 3\,234,25 + j 5\,897,75$$

$$= 18\,389,69 + j 19\,234,54$$

$$= 26\,611,055 \angle 46,286 \checkmark$$

$$V_s \text{ line voltage} = \sqrt{3} \times 26\,611,055 = 46\,091,69 \text{ kV} \checkmark \quad (5)$$

4.2.2      Reg =  $\frac{V_s - V_r}{V_r}$

$$= \frac{26611,055 - 20207,26}{20207,26} \quad \checkmark \quad 35000 / \sqrt{3} = 20207,26$$

$$= 0,317 \text{ p.u.} \checkmark$$

OR ALTERNATE

$$\text{Reg} = \frac{V_s - V_r}{V_r}$$

$$= \frac{46091,69 - 35000}{35000}$$

$$= 0,317 \text{ p.u.} \quad (2)$$

$$4.2.3 \quad \text{Output} = 1,73 \text{ MW}/3 \text{ per phase} = 576,67 \text{ kW} \checkmark$$

$$\text{Power loss} = I^2 R$$

$$= (38,05)^2 \times 85$$

$$= 123,06 \text{ kW} \checkmark$$

$$\text{Input} = \text{output} + \text{losses}$$

$$= 576,67 + 123,06$$

$$= 699,73 \text{ kW} \checkmark$$

$$\text{Efficiency} = \frac{\text{output}}{\text{Input}}$$

$$= \frac{576,67}{699,73} \checkmark$$

$$= 0,824 \quad (82,4 \% ) \checkmark$$

(5)  
[20]**QUESTION 5**

- 5.1 Sudden changes of load on synchronous motors sometimes set up oscillations that are superimposed upon the normal rotation giving rise to periodic variations in speed of a very low frequency.  $\checkmark$  (2)

- 5.2 5.2.1 Slip-ring motor VL = 95

$$E_o = \frac{95}{\sqrt{3}} = 54,85 \text{ V} \quad (\text{star rotor}) \checkmark$$

$$Z_o = 0,7 + j 9$$

$$Z_{st} = 4 + j 7$$

$$\text{Starting } Z_o = (0,7 + j 9) + (4 + j 7) \checkmark$$

$$= 4,7 + j 16$$

$$= 16,68 \angle 73,63 \quad \checkmark$$

$$I_o = \frac{E_o}{Z_o} = \frac{54,85}{16,68} = 3,29 \text{ A} \checkmark$$

(4)

$$5.2.2 \quad E_2 = s E_0 = (0,05) (54,85) = 2,74$$

$$X_2 = s X_0 = (0,05) (9) = 0,45$$

$$Z_2 = \sqrt{(R_2)^2 + (X_2)^2}$$

$$= \sqrt{(0,7)^2 + (0,45)^2} = 0,83 \checkmark$$

$$I_2 = \frac{E_2}{Z_2} = \frac{2,74}{0,83} = 3,3 \text{ A} \checkmark \quad (2)$$

$$5.3 \quad 5.3.1 \quad E_0 = 145/\sqrt{3} = 83,72 \text{ V} \checkmark$$

$$I_2 = \frac{E_0}{Z_0}$$

$$= \frac{83,72}{\sqrt{(R_2)^2 + (X_0)^2}} \checkmark$$

$$= \frac{83,72}{\sqrt{(1,25)^2 + (6,75)^2}} \checkmark$$

$$= \frac{83,72}{6,86}$$

$$= 12,2 \text{ A} \checkmark \quad (4)$$

$$5.3.2 \quad \tan \Phi = \frac{X_0}{R_2} = \frac{6,75}{1,25} = 5,4 \checkmark$$

$$\Phi = 79,51$$

$$\cos \Phi = 0,182 \checkmark \quad (2)$$

$$5.4 \quad 5.4.1 \quad f = \frac{np}{60}$$

$$P = \frac{60 \times 60}{1200} = 3 \checkmark$$

$$\text{poles} = 6 \checkmark \quad (2)$$

5.4.2 8 = slots / pole / phase

$$= \text{slots} / 6 / 3 \quad \checkmark$$

$$\text{slots} = 8 \times 6 \times 3 = 144$$

$$Z = 144 \times 6 = 864 \quad \checkmark$$

$$E_p = 2,22 k_d k_p \Phi f Z / \text{phase}$$

$$\frac{885}{\sqrt{3}} \quad \checkmark = 2,22 (0,96) (1) \Phi (60) \left( \frac{864}{3} \right) \quad \checkmark$$

$$\Phi = 0,0139 \text{ Wb.} \quad \checkmark$$

(4)  
[20]

**TOTAL: 100**