



**higher education
& training**

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE

NATIONAL CERTIFICATE

NOVEMBER EXAMINATION

ELECTROTECHNICS N5

24 NOVEMBER 2016

This marking guideline consists of 9 pages.

QUESTION 1

- 1.1 No. ✓
At no-load the field flux is too small to allow the build-up of the necessary back EMF which causes the motor to speed up towards infinity until it burns out completely. ✓ (2)
- 1.2 Back EMF is the voltage which is generated due to the armature conductors moving through the magnetic field flux. ✓
This voltage is in opposition to the applied voltage by which it is generated. ✓
The motor will speed up until the necessary back EMF is built up because a low back EMF will cause a high armature current which will supply the extra driving torque to speed up the armature. ✓ Any change in the back EMF will result in a change of speed. The back EMF acts like a governor and therefore the motor is self-regulating. ✓ (4)
- 1.3 Pole = 6 p = 3
c = 2p = 2 × 3 = 6 ✓ Z = 600
$$\frac{\text{Pole arc}}{\text{Pole pitch}} = 0,8$$

I = 790 A
At / p = $\frac{IZ}{2c} \times \frac{\text{Pole arc}}{\text{Pole pitch}}$
= $\frac{790 \times 600}{2 \times 6} \times 0,8$ ✓✓
= 5266,67 At ✓
Say 5267 At (4)
- 1.4 I = $\frac{88000}{435}$ = 202,3A ✓
At / p for full load = 10,5 A × 1800 t/p ✓ = 18900 At / p ✓
t / p for no load = 6,5 A × 1800 t/p ✓ = 11700 At / p ✓
At / p for series winding = 18900 – 11700 ✓
No of series t/p = 7200 At / p ✓
= 7200 / 202,3
= 35,6 ✓
Say 36 (8)

1.5 Lap windings are used in low-voltage and high-current machines. (1)

Wave windings are used in high-voltage and low-current machines. (1)
[20]

QUESTION 2

$$2.1 \quad C_1 = 380 \times 10^{-12} \text{ F} \quad (I \text{ max})$$

$$C_2 = 350 \times 10^{-12} \text{ F} \quad (I_2 = 0,707 I \text{ max})$$

$$X_{C1} = 1/2\pi f C_1 = \frac{1 \times 10^{12}}{2\pi \times 0,84 \times 10^6 \times 380} = 498,6 \Omega \quad \checkmark$$

$$X_{L1} = X_{C1} = 498,6 \quad (\text{resonance}) \quad \checkmark$$

$$X_{L1} = 2\pi f L$$

$$L = \frac{X_{L1}}{2\pi f} = \frac{498,6}{2\pi \times 0,84 \times 10^6} = 94,47 \mu\text{H} \quad \checkmark$$

$$X_{C2} = 1/2\pi f C_2 = \frac{10^{12}}{2\pi \times 0,84 \times 10^6 \times 350} \quad \checkmark = 541,34 \Omega \quad \checkmark$$

$$\text{Increase in } X_C = 541,34 - 498,6 = 42,74 \Omega \quad \checkmark$$

$$Z_2^2 = R^2 + (42,74)^2 \quad \checkmark$$

$$Z_2 = \sqrt{R^2 + (42,74)^2}$$

$$I_1 = V/Z_1$$

$$I_2 = 0,707 I_1 = 0,707 V/Z_1 = V/Z_2$$

$$Z_1 = R \quad (\text{resonance})$$

$$0,707 V/Z_1 = V/Z_2$$

$$0,707 V/R = \frac{V}{\sqrt{R^2 + (42,74)^2}}$$

$$(0,707 V/R)^2 = \left[\frac{V}{\sqrt{R^2 + (42,74)^2}} \right]^2 \quad \checkmark$$

$$\frac{(0,707 V)^2}{R^2} = \frac{V^2}{R^2 + (42,74)^2}$$

$$\frac{R^2 + (42,74)^2}{R^2} = \frac{V^2}{(0,707 \text{ V})^2}$$

$$1 + \frac{(42,74)^2}{R^2} = \frac{1}{(0,707)^2} \checkmark$$

$$\frac{(42,74)^2}{R^2} = \frac{1}{(0,707)^2} - 1 = 1,001$$

$$R^2 = \frac{(42,74)^2}{1,001}$$

$$R = 42,7 \text{ ohms} \quad \checkmark \quad (10)$$

2.2 2.2.1 $X_L = 2 \pi f L$
 $= 2 \pi \times 3 \times 10^6 \times 375 \times 10^{-6} \checkmark = 7068,58 \Omega \checkmark$

$f(\text{res}) = 1 / 2 \pi \sqrt{LC}$
 $3 \times 10^6 = 1 / 2 \pi \sqrt{375 \times 10^{-6} \times C} \checkmark$
 $\sqrt{375 \times 10^{-6} \times C} = 1 / 2 \pi 10^6 \times 3 \quad \checkmark$
 $375 \times 10^{-6} \times C = (1 / 2 \pi 10^6 \times 3)^2 \quad \checkmark$
 $C = 7,49 \times 10^{-12} \text{ F} \quad \checkmark \quad (5)$

2.2 2.2.2 $Z_{\text{parallel}} = L/CR$
 $= \frac{375 \times 10^{-6}}{7,49 \times 10^{-12} \times 33} \checkmark$
 $= 1517,174 \text{ k}\Omega \quad \checkmark \quad (2)$

2.2.3 $I = V/Z_T$
 $= 120 / 6400 + 1517174$
 $= 120 / 1523574$
 $= 0,079 \text{ mA}$

pd across coil $= 0,079 \times 10^{-3} \times 1517174 = 119,857 \text{ V} \quad \checkmark$

$I_{\text{coil}} = 119,857 / \sqrt{(33)^2 + (7068,58)^2}$
 $= 16,4 \text{ mA} \quad \checkmark$

$I_{\text{cap}} = 2 \times 3,14 \times 2,2 \times 10^6 \times 15 \times 10^{-12} \times 79,34$
 $= 16,4 \text{ mA} \quad \checkmark \quad (3)$

[20]

QUESTION 3

- 3.1
- Making the transformer window long and narrow
 - Arranging the primary and secondary windings concentrically
 - Sandwiching the primary and secondary windings
 - Using shell-type construction
- (4)

3.2 3.2.1 $S = 2800 < 0 \times 1000 < -36,87$
 $= 2800 < -36,87 \quad \text{kVA} \quad \checkmark$

TRF A

$$P = I V \cos \phi$$

$$20000 = 380 \times 330 \times \cos \phi$$

$$\cos \phi = 0,159$$

$$\phi = 80,85 \quad \checkmark$$

$$I_a = 380 < -80,85$$

$$Z_A = \frac{V}{I} = \frac{330 < 0}{380 < -80,85} = 0,868 < 80,85$$

$$\checkmark$$

$$= 0,138 + j 0,857$$

TRF.B

$$P = I V \cos \phi$$

$$25000 = 380 \times 180 \times \cos \phi$$

$$\cos \phi = 0,365$$

$$\phi = 68,59$$

$$I_B = 380 < -68,59 \quad \checkmark$$

$$Z_B = \frac{V}{I} = \frac{180 < 0}{380 < -68,59} = 0,47 < 68,59 \quad \checkmark$$

$$= 0,17 + j 0,44$$

$$Z_A + Z_B = 0,138 + j 0,857 + 0,17 + j 0,44$$

$$= 0,31 + j 1,3$$

$$= 1,34 < 76,59 \quad \checkmark$$

$$Z_T = \frac{Z_A \times Z_B}{Z_A + Z_B} = \frac{0,868 < 80,85 \times 0,47 < 68,59}{1,34 < 76,59}$$

$$= 0,3 < 72,85 \quad \checkmark$$

$$V_D = I_L \times Z_T$$

$$= 1000 < -36,87 \times 0,3 < 72,85$$

$$= 300 < 35,98 \quad \checkmark = 242,77 + j176,25$$

$$V_S = V(\text{NO LOAD}) - V_D \quad \checkmark$$

$$= 2800 < 0 - 300 < 35,98$$

$$= (2800 + j0) - (242,77 + j176,25) = 2800 + j0 - 242,77 - j176,25$$

$$= 2557,23 - j176,25$$

$$= 2563,3 < -3,94 \quad \checkmark \quad (10)$$

$$3.2.2 \quad S = V_S \times I(\text{LOAD})$$

$$= 2563,3 < -3,94 \times 1000 < -36,87$$

$$= 2563,3 < -40,8 \text{ kVA} \quad \checkmark$$

$$S_A = \frac{S \times Z_B}{Z_A + Z_B} = \frac{2563,3 < -40,8 \times 0,47 < 68,59}{1,34 < 76,59}$$

$$= 899,07 < -48,8 \text{ kVA} \quad \checkmark$$

$$\text{COS } \phi = 0,66 \text{ lagging} \quad \checkmark \quad (3)$$

$$3.2.3 \quad S_B = \frac{S \times Z_A}{Z_A + Z_B} = \frac{2563,3 < -40,8 \times 0,868 < 80,85}{1,34 < 76,59}$$

$$= 1660,4 < -36,54 \text{ kVA} \quad \checkmark$$

$$\text{COS } \phi = 0,8 \text{ lagging} \quad \checkmark \quad (3)$$

[20]

QUESTION 4

4.1 Loop resistance $= \frac{\rho l}{a}$
 $= \frac{1,7 \times 62 \times 10^5}{10^6 \times \pi \times 0,8^2} \checkmark$
 $= 5,24 \Omega \checkmark$

Loop inductance $= 62 [0,05 + 0,2 \log_e d/r] \text{ mH} \checkmark$
 $= 62 [0,05 + 0,2 \log_e (90/0,8)] \text{ mH} \checkmark$
 $= 61,66 \text{ mH} \checkmark$

Total capacitance $= \frac{31}{36 \log_e \left(\frac{d-r}{r} \right)}$
 $= \frac{31}{36 \log_e \left(\frac{90 - 0,8}{0,8} \right)} \checkmark \checkmark$
 $= 0,1918 \mu\text{F} \checkmark \quad (8)$

4.2 Total input power $= \frac{21500}{0,8} = 26875 \text{ W} \checkmark$

$P_1 + P_2 = 26875 \checkmark \quad \dots\dots \text{eqn. (1)}$

$\text{Tan } \phi = \frac{\sqrt{3} (P_2 - P_1)}{26875}$

$P_2 - P_1 = \frac{26875}{\sqrt{3}} \frac{\sqrt{1 - \cos^2 \phi}}{\cos \phi} \checkmark$
 $= \frac{26875}{\sqrt{3}} \frac{\sqrt{1 - 0,7^2}}{0,7} \checkmark$
 $= 15829,78 \text{ W} \checkmark \quad \dots\dots \text{eqn. (2)}$

$(1) + (2) = 2 \times P_2 = 42704,78 \text{ W} \checkmark$

$P_2 = 21352,39 \text{ W} \checkmark$

Sub in (eqn. 1) $P_1 = 26875 - 21352,39$
 $= 5522,6 \text{ W} \checkmark \quad (8)$

$$\begin{aligned}
 4.3.1 \quad W T &= W 1 + W 2 \\
 &= 735 + 390 \\
 &= 1125 \text{ kW} \quad \checkmark
 \end{aligned}
 \tag{1}$$

$$\begin{aligned}
 4.3.2 \quad \text{Tan } \phi &= \sqrt{3} \left(\frac{W1 - W2}{W1 + W2} \right) \\
 &= \sqrt{3} \left(\frac{735 - 390}{735 + 390} \right) \quad \checkmark \\
 &= \sqrt{3} \left(\frac{345}{1125} \right) \\
 &= 0,53 \quad \checkmark \\
 \phi &= 27,92 \\
 \cos \phi &= 0,88 \quad \checkmark
 \end{aligned}
 \tag{3}$$

[20]

QUESTION 5

5.1 No. ✓
If the rotor were to run at synchronous speed, there would be no relative speed difference between the rotating magnetic field and the rotor ✓, and hence no emf will be induced in the rotor ✓ and therefore there will be no rotor current and no torque either. ✓

(4)

5.2 5.2.1 $X_s = 9,6 \Omega$ per phase $\theta = 30$
 $V_P = 3430 \text{ V}$

$$\begin{aligned}
 E_Z &= j E A - (E B \sin \theta + j E B \cos \theta) \quad \checkmark \\
 &= j 3430 - (3430 \sin 30 + j 3430 \cos 30) \\
 &= j 3430 - 1715 - j 2970,47 \quad \checkmark \\
 &= - 1715 + j 459,53 \\
 &= 1775,5 \text{ V} \quad \checkmark
 \end{aligned}$$

$$\begin{aligned}
 \text{Circulating I} &= \frac{E_z}{2X_s} = \frac{1775,5}{2 \times 9,6} \quad \checkmark \\
 &= 92,47 \text{ A} \quad \checkmark
 \end{aligned}
 \tag{5}$$

$$\begin{aligned}
 5.2.2 \quad \text{Terminal V/ P} &= E_a \cos \frac{\theta}{2} \\
 &= 3430 \cos 15^\circ \checkmark \\
 &= 3313,13 \text{ V} \checkmark \quad (2)
 \end{aligned}$$

$$\begin{aligned}
 5.2.3 \quad P &= \sqrt{3} I_L V_L \\
 V_L &= \sqrt{3} V_P \\
 &= \sqrt{3} \times 3313,13 \\
 &= 5738,5 \text{ V} \checkmark \\
 &= \sqrt{3} \times 92,47 \times 5738,5 \text{ W} \checkmark \\
 &= 919,093 \text{ kW} \checkmark \quad (3)
 \end{aligned}$$

$$\begin{aligned}
 5.3 \quad 5.3.1 \quad V_L = 520 \quad N = 1000 \text{ r/min} \quad f = 50 \\
 f &= N p / 60 \\
 50 &= \frac{1000 \times p}{60} \\
 p &= 3 \quad \checkmark \\
 \text{no of poles} &= 3 \times 2 = 6 \quad \checkmark \quad (2)
 \end{aligned}$$

$$\begin{aligned}
 5.3.2 \quad \text{No of slots per phase} &= 2 \times 6 = 12 \\
 \text{No of conductors per phase} &= 12 \times 4 \\
 &= 48 \quad \checkmark \\
 \text{EMF per phase} &= \frac{645}{\sqrt{3}} \\
 &= 372,4 \quad \checkmark \\
 E_p &= 2,22 k_d k_p \phi f Z / p_h \\
 372,4 &= 2,22 \times 0,96 \times 1 \times \phi \times 50 \times 48 \quad \checkmark \\
 \phi &= \frac{372,4}{2,22 \times 0,96 \times 1 \times 50 \times 48} \\
 \phi &= 0,073 \text{ Wb} \\
 &= 73 \text{ mWb} \quad \checkmark \quad (4)
 \end{aligned}$$

[20]

TOTAL: 100